

## Lab 6


### Calculations:

Assuming worst case delay on all full adders, best clk frequency


Worst case delay assuming last carryout = don't care:  $16.83 \times 10^{-10} \text{s}$

Frequency for DFF holding accurate values =  $1/16.83 \times 10^{-10} \text{s} = 5.94 \text{MHz}$


### Ripple Carry Adder Screenshot:

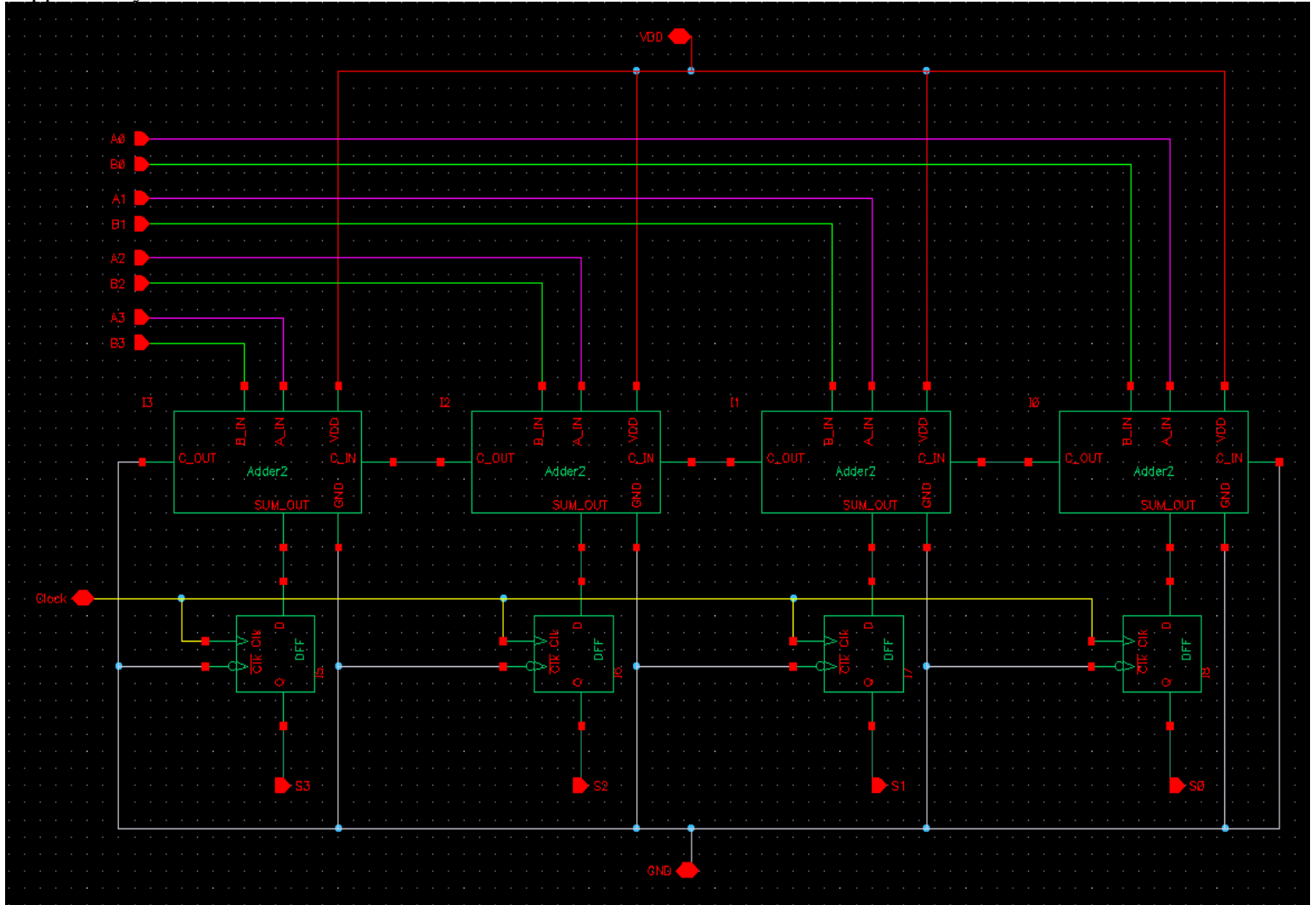


D Flip Flop Screenshot:

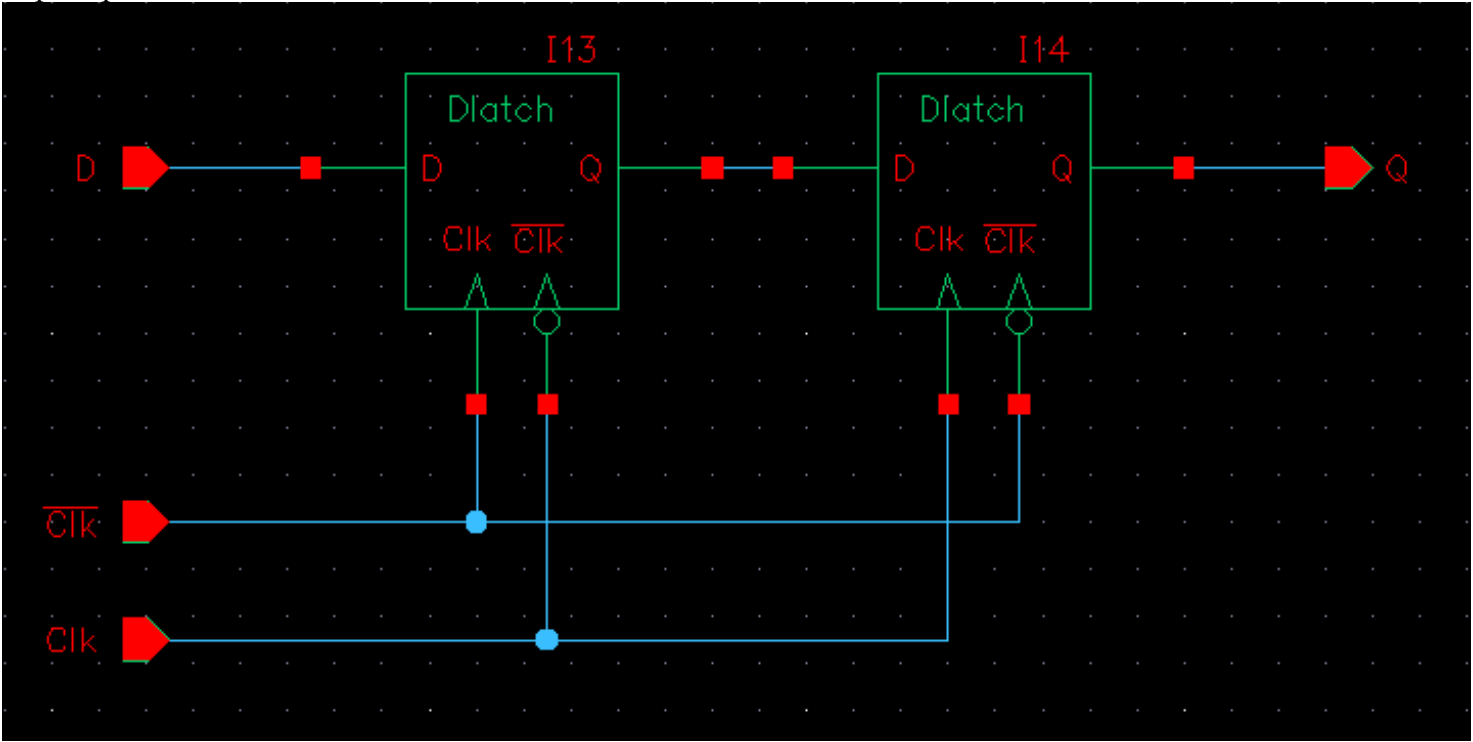


Carry look-ahead full adder:

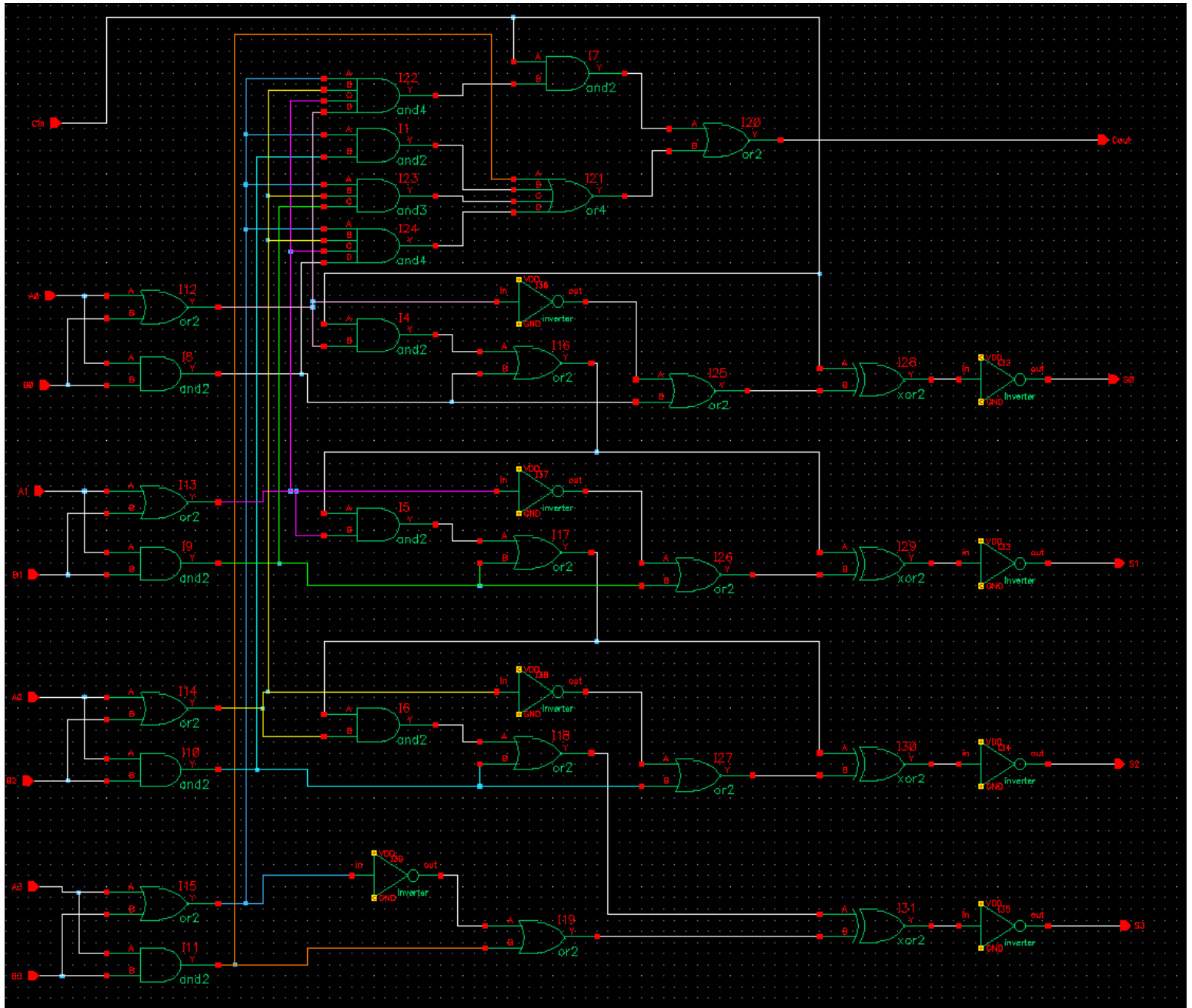


And4:

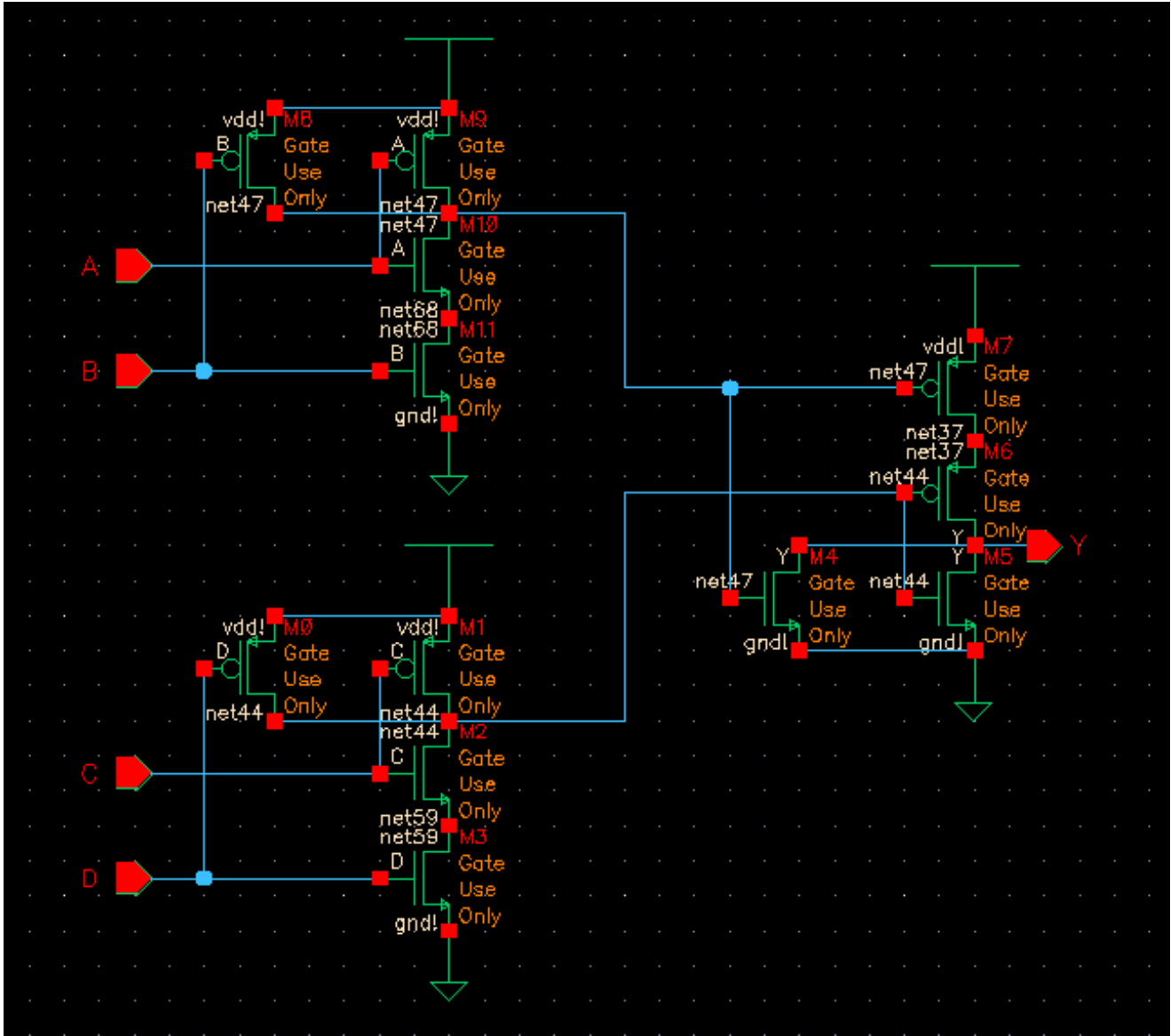


And3:

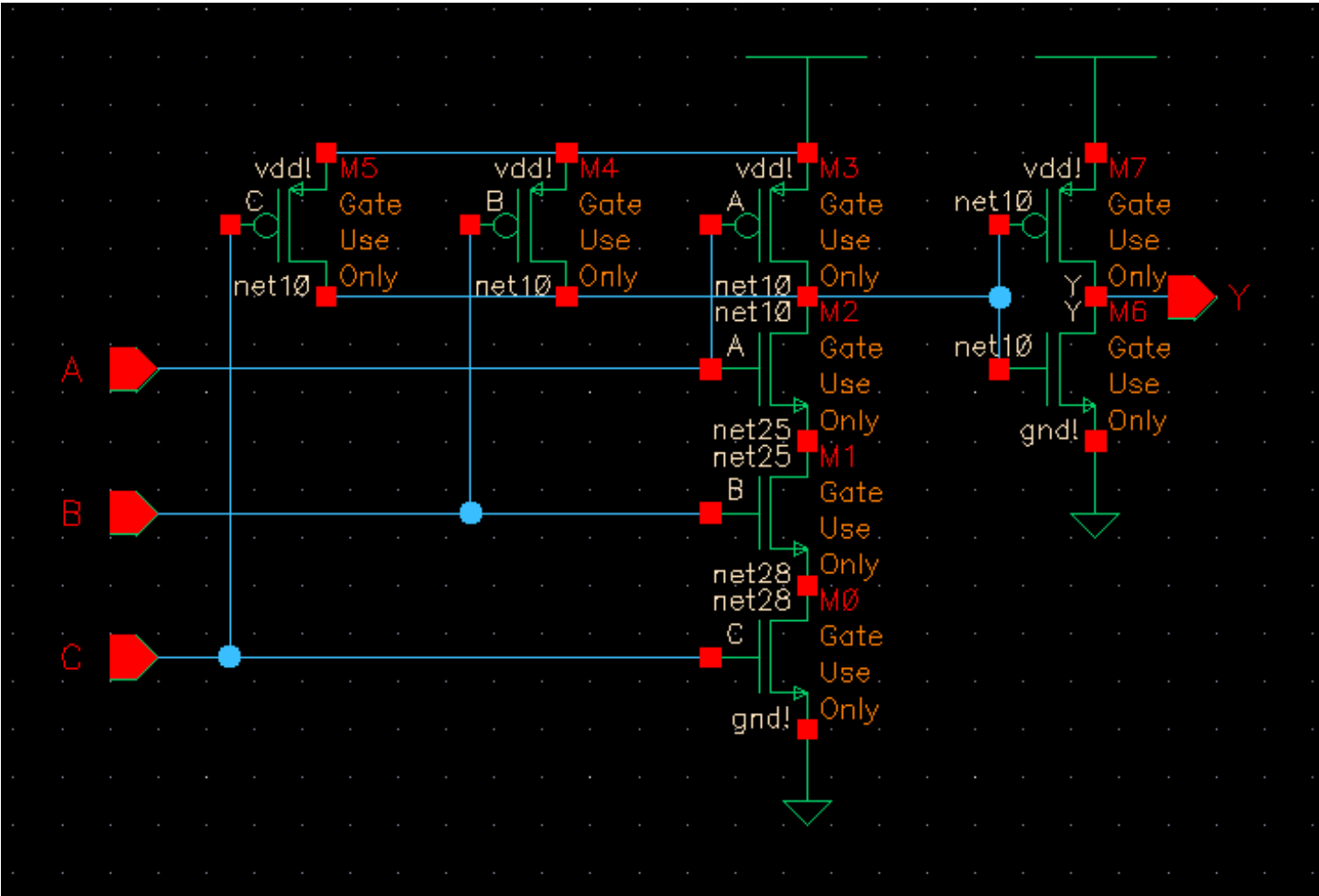


And2:

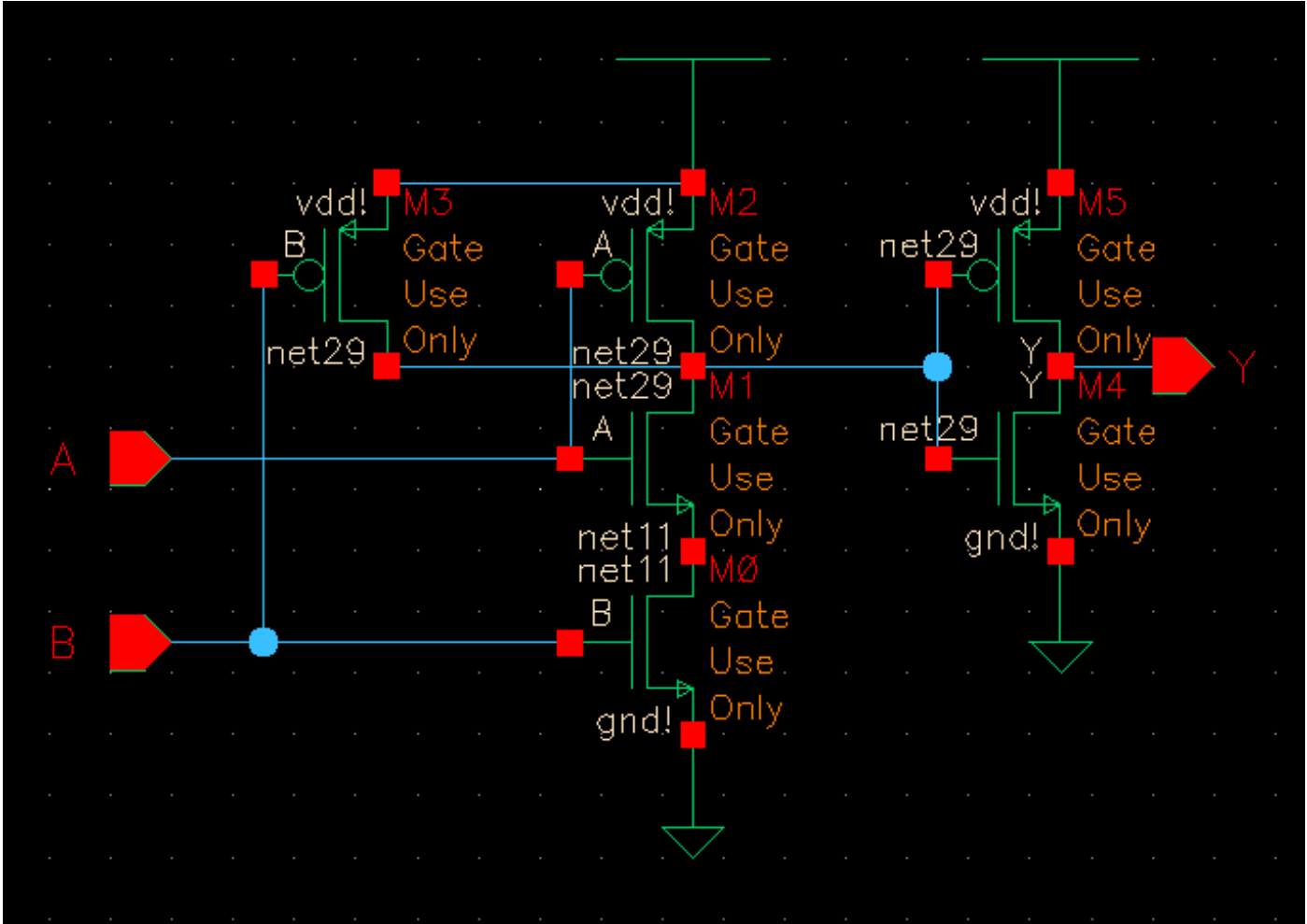


Or4:

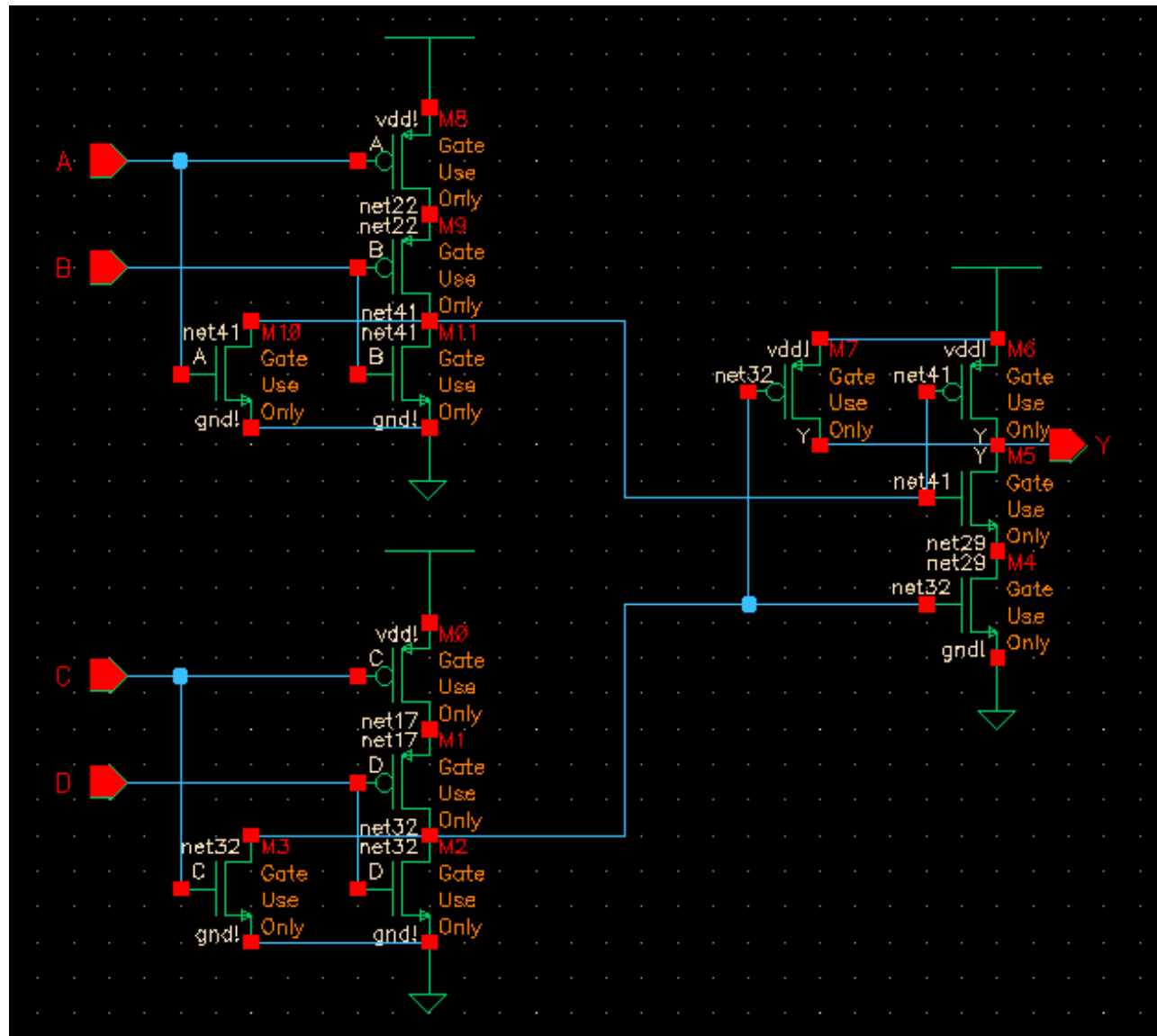

Or2:

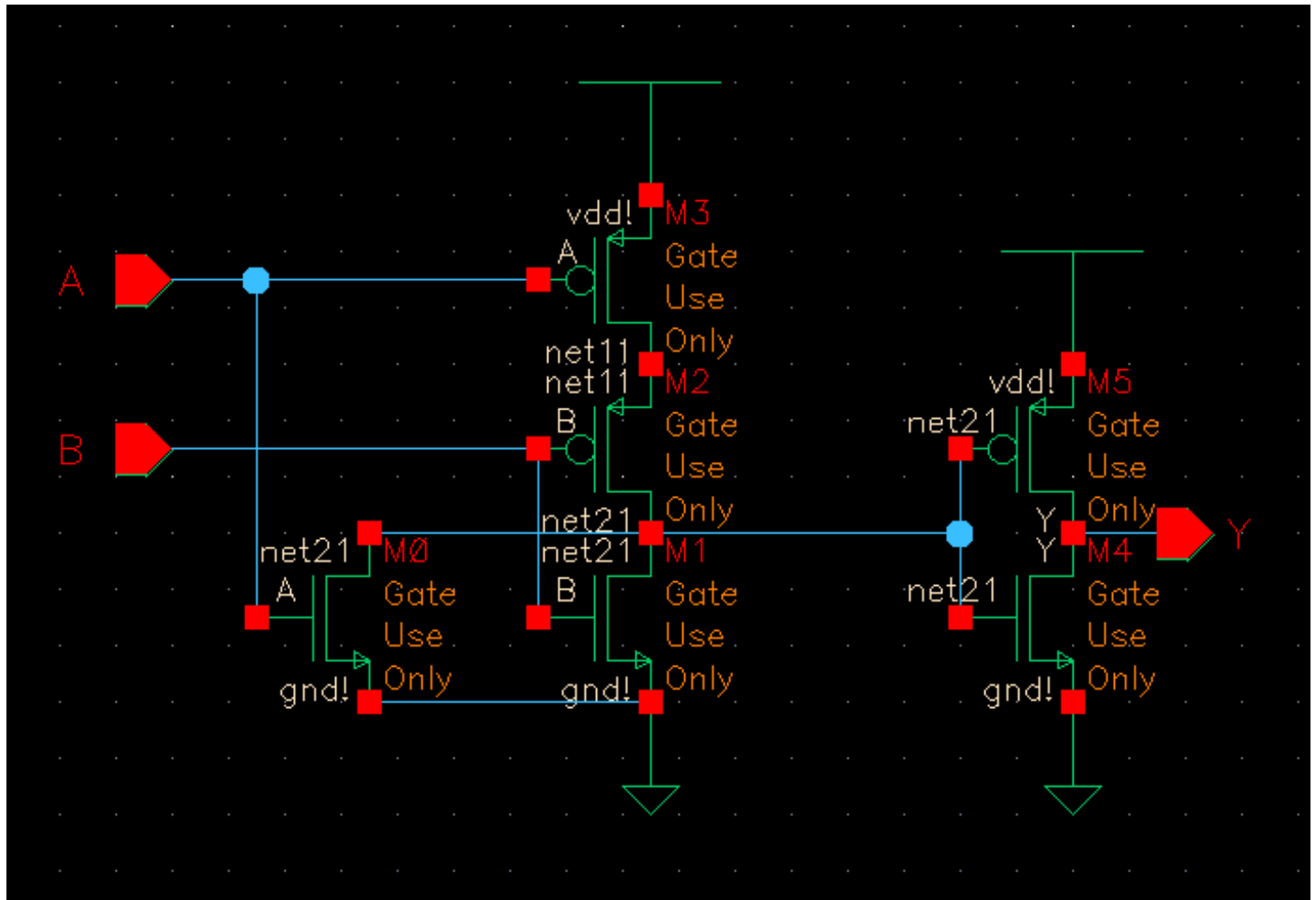

Xor2:

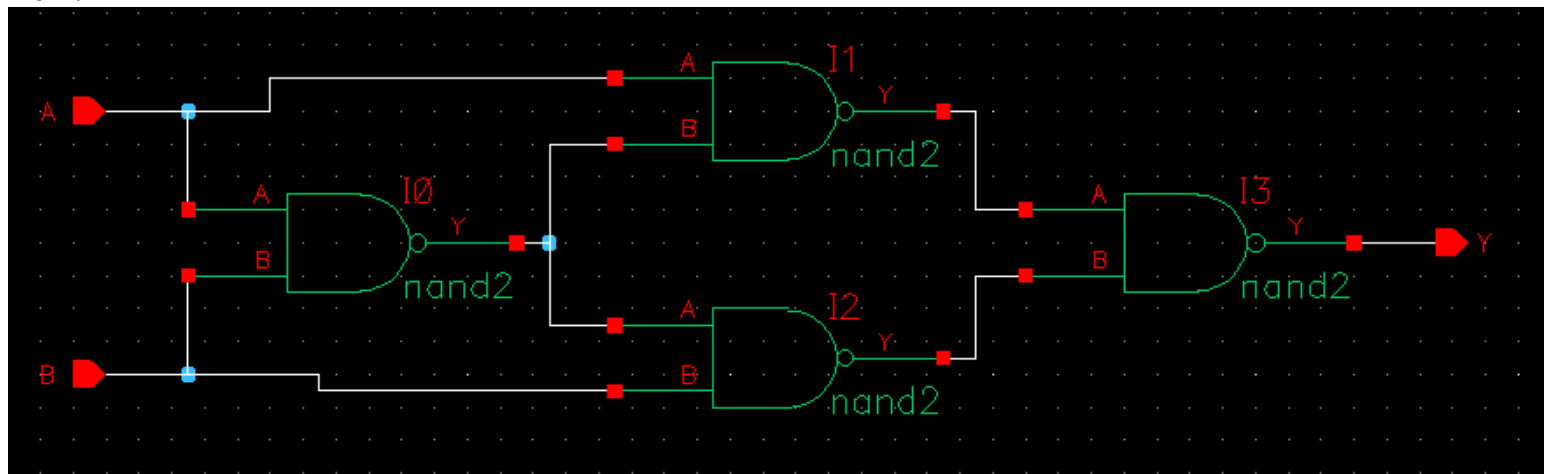



Nor2:

 


Table of Values:

	Ripple Carry Adder	Carry Look-ahead Adder
Clock Frequency @Vdd=2.5V	594Mhz	1.34Ghz

Static Power	1.01E-08W	1.30E-05W
Dynamic Power	7.70E-09W	2.59E-06W